


## Sistemas Digitais I

LESI - 2º ano

### Lesson 3 - Boolean Algebra

Prof. João Miguel Fernandes  
(miguel@di.uminho.pt)

Dept. Informática

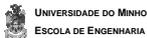

## 3. Boolean Algebra

- Introduction -

- The success of computer technology is primarily based on simplicity of designing digital circuits and ease of their manufacture.
- Digital circuits are composed of basic processing elements, called gates, and basic memory elements, called flip-flops.
- The simplicity in digital circuit design is due to the fact that input and output signals of each gate or flip-flop can assume only two values, 0 and 1.
- The changes in signal values are governed by laws of Boolean algebra.
- The fact that Boolean algebra is finite and richer in properties than ordinary algebra leads to simple optimisation techniques for functions.
- In order to learn techniques for design of digital circuits, we must understand the properties of Boolean algebra.

## 3. Boolean Algebra

- Binary Signals (1) -

- Digital logic hides the analog world by mapping the infinite set of real values into 2 subsets (0 and 1).
- A logic value, 0 or 1, is often called a **binary digit (bit)**.
- With  $n$  bits,  $2^n$  different entities are represented.
- When using electronic circuits, digital designers often use the words "LOW" and "HIGH", in place of "0" and "1".
- The assignment of 0 to LOW and 1 to HIGH is called **positive logic**. The opposite assignment is called **negative logic**.
- Other technologies can be used to represent bits with physical states.

## 3. Boolean Algebra

- Binary Signals (2) -

Technology	State Representation (Bit)	
	0	1
Practical logic	Fixed at low potential	Fixed at high potential
Relay logic	Circuit open	Circuit closed
Complementary metal-oxide semiconductor (CMOS) logic	0-4.5V	5.5-9.5V
Transistor-transistor logic (TTL)	0-0.5V	2.0-3.0V
Photo-optics	Light off	Light on
Domestic memory	Capacitor discharged	Capacitor charged
Mechanical, reusable memory	Electromagnet pulled	Electromagnet released
Digital read-only memory	Plate closed	Plate raised
Bubble memory	No magnetic bubble	Bubble present
Magnetic tape or disk	Flux direction "no flux"	Flux direction "north"
Programmable memory	No level in state A	Not stable in state B
Read-only compact disc	No pit	Pit
Re-writable compact disc	Optically transparent	Optically non-transparent

## 3. Boolean Algebra


- Combinational vs. Sequential Systems -

- A **combinational** logic system is one whose outputs depend only on its current inputs.
- A combinational system can be described by a **truth table**.
- The outputs of a **sequential** logic circuit depend not only on the current inputs but also on the past sequence of inputs  $\Rightarrow$  memory.
- A sequential system can be described by a **state table**.
- A combinational system may contain any number of logic gates but no feedback loops.
- A **feedback loop** is a signal path of a circuit that allows the output of a gate to propagate back to the input of that same gate.
- Feedback loops generally create sequential circuit behaviour.
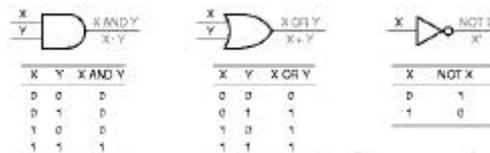
## 3. Boolean Algebra

- Gates (1) -

- Three basic gates (AND, OR, NOT) are sufficient to build any combinational digital logic system. They form a complete set.




- The symbols and truth tables for AND and OR may be extended to gates with any number of inputs.
- The **bubble** on the inverter output denotes "inverting" behaviour.
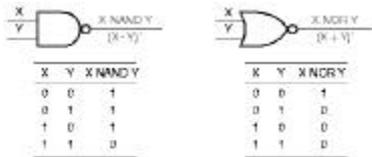
### 3. Boolean Algebra

- Gates (2) -

- Two more logic functions are obtained by combining NOT with an AND or OR function in a single gate.



- The symbols and truth tables for NAND and NOR may also be extended to gates with any number of inputs.

### 3. Boolean Algebra

- Switching Algebra -

- In 1854, G. Boole (1815-1865) introduced the formalism that we use for the systematic treatment of logic which is now called Boolean Algebra.



- In 1938, C. Shannon (1916-2001) applied this algebra to prove that the properties of electrical switching circuits can be represented by a 2-valued Boolean Algebra, which is called Switching Algebra.



- Using this algebra, one can formulate propositions that are true or false, combine them to make new propositions and determine if the new propositions are true or false.
- We use a symbolic variable (ex. X) to represent the condition of a logic signal, which is in one of two possible values ("0" or "1").

### 3. Boolean Algebra

- Axioms (1) -

- The axioms (or postulates) of a mathematical system are a minimal set of basic definitions that we assume to be true.
- The first axioms embody the digital abstraction:  
(A1)  $X=0$  if  $X \neq 1$       (A1')  $X=1$  if  $X \neq 0$
- We stated these axioms as a pair, the only difference being the interchange of the symbols 0 and 1.
- This applies to all the axioms and is the basis of duality.
- The next axioms embody the complement notation:  
(A2) If  $X=0$ , then  $X'=1$       (A2') If  $X=1$ , then  $X'=0$



- We use a prime (') to denote an inverter's function.

### 3. Boolean Algebra

- Axioms (2) -

- The last three pairs of axioms state the formal definitions of the AND (logical multiplication) and OR (logical addition) operations:  
(A3)  $0 \cdot 0 = 0$       (A3')  $1 + 1 = 1$   
(A4)  $1 \cdot 1 = 1$       (A4')  $0 + 0 = 0$   
(A5)  $0 \cdot 1 = 1 \cdot 0 = 0$       (A5')  $1 + 0 = 0 + 1 = 1$



- By convention, in a logic expression involving both multiplication and addition, multiplication has precedence.
- The expression  $X \cdot Y + Y \cdot Z'$  is equivalent to  $(X \cdot Y) + (Y \cdot Z')$ .
- The axioms (A1-A5, A1'-A5') completely define Boolean algebra.

### 3. Boolean Algebra

- Theorems (1) -

- Theorems are statements, known to be true, that allow us to manipulate algebraic expressions to have simpler analysis or more efficient synthesis of the corresponding circuits.
- Theorems involving a single variable:  
(T1)  $X+0 = X$       (T1')  $X \cdot 1 = X$       (Identities)  
(T2)  $X+1 = 1$       (T2')  $X \cdot 0 = 0$       (Null elements)  
(T3)  $X+X = X$       (T3')  $X \cdot X = X$       (Idempotency)  
(T4)  $(X')' = X$       (Involution)  
(T5)  $X+X' = 1$       (T5')  $X \cdot X' = 0$       (Complements)
- These theorems can be proved to be true. Let us prove T1:  
[X=0]  $0+0=0$  (true, according to A4)  
[X=1]  $1+0=1$  (true, according to A5)

### 3. Boolean Algebra

- Theorems (2) -

- Theorems involving two or three variables:  
(T6)  $X+Y = Y+X$       (T6')  $X \cdot Y = Y \cdot X$       (Commutativity)  
(T7)  $(X+Y)+Z = X+(Y+Z)$       (T7')  $(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$       (Associativity)  
(T8)  $X \cdot Y + X \cdot Z = X \cdot (Y+Z)$       (T8')  $(X+Y) \cdot (X+Z) = X+Y \cdot Z$       (Distributivity)  
(T9)  $X+X \cdot Y = X$       (T9')  $X \cdot (X+Y) = X$       (Covering)  
(T10)  $X \cdot Y + X \cdot Y' = X$       (T10')  $(X+Y) \cdot (X+Y') = X$       (Combining)  
(T11)  $X \cdot Y + X' \cdot Z + Y \cdot Z = X \cdot Y + X' \cdot Z$       (Consensus)  
(T11')  $(X+Y) \cdot (X'+Z) \cdot (Y+Z) = (X+Y) \cdot (X'+Z)$
- Attention to theorem T8' which is not true for integers and reals.
- T9 and T10 are used in the minimisation of logic functions.

### 3. Boolean Algebra


- Theorems (3) -

- Several important theorems are true for an arbitrary number of variables.
- Theorems involving n variables:
  - (T12)  $X+X+ \dots +X = X$  Generalised Idempency
  - (T12)  $X \cdot X \cdot \dots \cdot X = X$
  - (T13)  $(X_1 \cdot X_2 \cdot \dots \cdot X_n)' = X_1' + X_2' + \dots + X_n'$  DeMorgan's theorems
  - (T13')  $(X_1 + X_2 + \dots + X_n)' = X_1' \cdot X_2' \cdot \dots \cdot X_n'$
  - (T14)  $[F(X_1, X_2, \dots, X_n, +, \cdot)]' = F(X_1', X_2', \dots, X_n', +, \cdot)$  Generalised DeMorgan's th.
  - (T15)  $F(X_1, X_2, \dots, X_n) = X_1 \cdot F(1, X_2, \dots, X_n) + X_1' \cdot F(0, X_2, \dots, X_n)$  Shannon's expansion theorems
  - (T15')  $F(X_1, X_2, \dots, X_n) = [X_1 + F(0, X_2, \dots, X_n)] \cdot [X_1' + F(1, X_2, \dots, X_n)]$
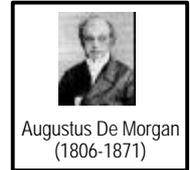
### 3. Boolean Algebra

- Theorems (4) -


- DeMorgan's theorem (T13 and T13') for n=2:
  - $(X \cdot Y)' = X' + Y'$
  - $(X + Y)' = X' \cdot Y'$
- DeMorgan's theorem gives a procedure for complementing a logic function.
- DeMorgan's theorem can be used to convert AND/OR expressions to OR/AND expressions.
- Example:
  - $Z = A' \cdot B' \cdot C + A' \cdot B \cdot C + A \cdot B' \cdot C + A \cdot B \cdot C'$
  - $Z' = (A + B + C) \cdot (A + B' + C) \cdot (A' + B + C) \cdot (A' + B' + C)$


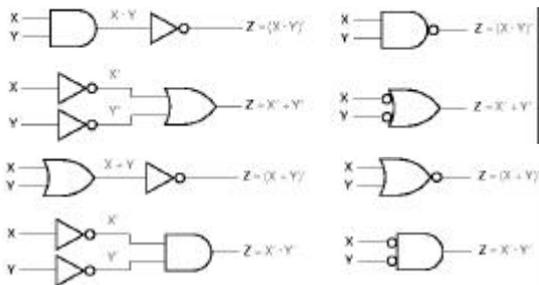
### 3. Boolean Algebra

- Theorems (5) -

Equivalent gates according to DeMorgan's theorem



### 3. Boolean Algebra

- Theorems (6) -

- Since Boolean algebra has only two elements, we can also show the validity of these theorems by using truth tables.
- To do this, a truth table is built for each side of the equation that appears in the theorem.
- Then both sides of the equation are checked to see if they yield identical results for all the combinations of variable values.
- Let us prove DeMorgan's theorem (T13 and T13') for n=2:
  - $(X+Y)' = X' \cdot Y'$
  - $(X \cdot Y)' = X' + Y'$

X	Y	X'	Y'	X'+Y'	X'·Y'
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

X	Y	X'	Y'	X'+Y'	X'·Y'
0	0	1	1	1	1
0	1	1	0	1	0
1	0	0	1	1	0
1	1	0	0	0	0


### 3. Boolean Algebra

- Duality (1) -

- Theorems were presented in pairs.
- The prime version of a theorem is obtained from the unprimed version by swapping "0" and "1", and "·" and "+".
- Principle of Duality:** Any theorem or identity in Boolean algebra remains true if 0 and 1 are swapped and · and + are swapped throughout.
- Duality is important because it doubles the usefulness of everything about Boolean algebra and manipulation of logic functions.
- The **dual** of a logic expression is the same expression with + and · swapped:  $F^D(X_1, X_2, \dots, X_n, +, \cdot) = F(X_1, X_2, \dots, X_n, \cdot, +)$ .
- Do not confuse duality with DeMorgan's theorems!
  - $[F(X_1, X_2, \dots, X_n, +, \cdot)]' = F(X_1', X_2', \dots, X_n', \cdot, +)$
  - $[F(X_1, X_2, \dots, X_n)]' = F^D(X_1', X_2', \dots, X_n')$

### 3. Boolean Algebra


- Duality (2) -

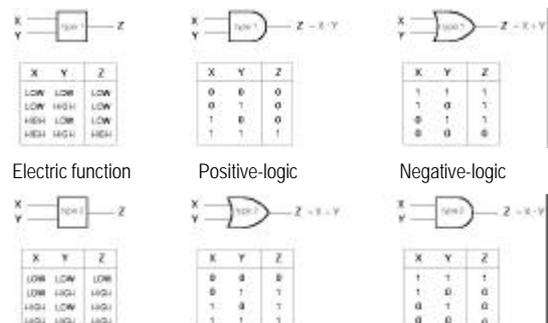


### 3. Boolean Algebra

- Duality (3) -

- Positive-logic

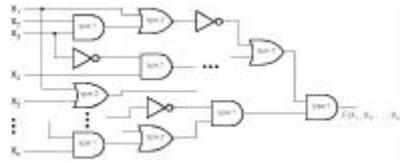

- Negative-logic

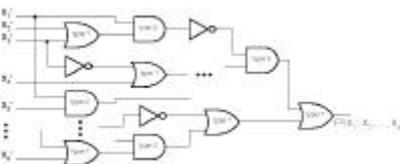

### 3. Boolean Algebra

- Standard Representation (1) -

- The most basic representation of a logic function is a truth table.
- A truth table lists the output of the circuit for every possible input combination.
- There are  $2^n$  rows in a truth table for an n-variable function.

Row	X	Y	Z	F
0	0	0	0	F(0,0,0)
1	0	0	1	F(0,0,1)
2	0	1	0	F(0,1,0)
3	0	1	1	F(0,1,1)
4	1	0	0	F(1,0,0)
5	1	0	1	F(1,0,1)
6	1	1	0	F(1,1,0)
7	1	1	1	F(1,1,1)

- There are  $2^8$  ( $8=2^3$ ) different logic functions for 3 variables.

### 3. Boolean Algebra

- Standard Representation (2) -

- Truth tables can be converted to algebraic expressions.
- A literal is a variable or the complement of a variable. Ex: X, Y, X'.
- A product term is a single literal or a logical product of two or more literals. Ex: Z, W·X·Y, W·X'·Y'.
- A sum-of-products (SOP) is a logical sum of product terms. Ex: Z' + W·X·Y.
- A sum term is a single literal or a logical sum of two or more literals. Ex: Z, W+X+Y, W+X'+Y'.
- A product-of-sums (POS) is a logical product of sum terms. Ex: Z' · (W+X+Y).

### 3. Boolean Algebra

- Standard Representation (3) -

- A normal term is a product or sum term in which no variable appears more than once. Examples (**non-normal** terms): W·X·X'·Z', W'+Y'+Z+W'.
- A n-variable minterm is a normal product term with n literals. Examples (with 4 variables): W·X·Y·Z', W'·X'·Y·Z.
- A n-variable maxterm is a normal sum term with n literals. Examples (with 4 variables): W+X+Y+Z', W'+X'+Y+Z.
- There is a correspondence between the truth table and minterms and maxterms.
- A minterm is a product term that is 1 in one row of the truth table.
- A maxterm is a sum term that is 0 in one row of the truth table.

### 3. Boolean Algebra

- Standard Representation (4) -

Minterms and maxterms for a 3-variable function F(X,Y,Z)

Row	X	Y	Z	F	Minterms	Maxterms
0	0	0	0	F(0,0,0)	X'·Y'·Z'	X+Y+Z
1	0	0	1	F(0,0,1)	X'·Y'·Z	X+Y+Z'
2	0	1	0	F(0,1,0)	X'·Y·Z'	X+Y'+Z
3	0	1	1	F(0,1,1)	X'·Y·Z	X+Y'+Z'
4	1	0	0	F(1,0,0)	X·Y'·Z'	X'+Y+Z
5	1	0	1	F(1,0,1)	X·Y'·Z	X'+Y+Z'
6	1	1	0	F(1,1,0)	X·Y·Z'	X'+Y'+Z
7	1	1	1	F(1,1,1)	X·Y·Z	X'+Y'+Z'

### 3. Boolean Algebra

- Standard Representation (5) -

- An n-variable minterm can be represented by an n-bit integer (the minterm number).
- In minterm i, a variable appears complemented if the respective bit in the binary representation of i is 0; otherwise it is uncomplemented.
- For example, row 5 (101) is related to minterm X·Y'·Z.
- In maxterm i, a variable appears complemented if the corresponding bit in the binary representation of i is 1; otherwise it is unprimed.
- For example, row 5 (101) is related to maxterm X'+Y+Z'.
- To specify the minterms and maxterms, it is mandatory to know the number of variables in the function and their order.

### 3. Boolean Algebra

- Standard Representation (6) -

- Based on the correspondence between the truth table and the minterms, an algebraic representation of a logic function can be created.
- The canonical sum of a logic function is a sum of the minterms corresponding to truth table rows for which the function is 1.
- From the table:  

$$F = \sum_{X,Y,Z} (0,3,4,6,7) = X \cdot Y \cdot Z' + X \cdot Y \cdot Z + X \cdot Y' \cdot Z' + X \cdot Y' \cdot Z + X \cdot Y \cdot Z$$
- The notation  $\sum_{X,Y,Z} (0,3,4,6,7)$  is a minterm list and means the sum of minterms 0,3,4,6, and 7, with variables X, Y, and Z.
- The minterm list is also known as the on-set for the logic function.

line	X	Y	Z	F
0	0	0	0	1
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	1
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

### 3. Boolean Algebra

- Standard Representation (7) -

- Based on the correspondence between the truth table and the maxterms, an algebraic representation of a logic function can be created.
- The canonical product of a function is a product of the maxterms corresponding to input combinations for which the function is 0.
- From the table:  

$$F = \prod_{X,Y,Z} (1,2,5) = (X+Y+Z) \cdot (X+Y'+Z) \cdot (X'+Y+Z)$$
- The notation  $\prod_{X,Y,Z} (1,2,5)$  is a maxterm list and means the product of maxterms 1,2, and 5, with variables X, Y, and Z.
- The maxterm list is also known as the off-set for the logic function.

line	X	Y	Z	F
0	0	0	0	1
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	1
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

### 3. Boolean Algebra

- Standard Representation (8) -

- It is easy to convert between a minterm list and a maxterm list.
- For a function of n variables, the minterms and maxterms are in the set  $\{0, 1, \dots, 2^n-1\}$ .
- A minterm or maxterm list contains a subset of these numbers.
- To switch between the lists, one takes the set complement.
- Examples:  

$$\sum_{A,B,C} (0,1,2,3) = \prod_{A,B,C} (4,5,6,7)$$

$$\sum_{X,Y} (1) = \prod_{X,Y} (0,2,3)$$

$$\sum_{W,X,Y,Z} (1,2,3,5,8,12,13) = \prod_{W,X,Y,Z} (0,4,6,7,9,10,11,14,15)$$

### 3. Boolean Algebra

- Standard Representation (9) -

- We have learned 5 possible representations for a combinational logic function.
  - A truth table;
  - An algebraic sum of minterms (the canonical sum);
  - A minterm list, using the  $\sum$  notation;
  - An algebraic product of maxterms (the canonical product);
  - A maxterm list, using the  $\prod$  notation;
- Each one of these representations specifies exactly the same information.
- Given any of them, we can derive the other four using a simple mechanical process.

### 3. Boolean Algebra

- Examples (1) -

- Ex.1: Let  $F = X \cdot Y + X \cdot Y' \cdot Z + X' \cdot Y \cdot Z$ . Derive the expression for  $F'$  in the product of sums form.  

$$F' = (XY + XY'Z + X'YZ)'$$

$$= (XY)' \cdot (XY'Z)'' \cdot (X'YZ)'$$

$$= (X'+Y') \cdot (X'+Y+Z') \cdot (X+Y'+Z')$$
- Ex.2: Express the function  $G(X,Y,Z) = X + Y \cdot Z$  as a sum of minterms.  

$$G = X + Y \cdot Z$$

$$= X \cdot (Y+Y') \cdot (Z+Z') + Y \cdot Z \cdot (X+X')$$

$$= XYZ + XYZ' + XY'Z + XY'Z' + XYZ + X'YZ$$

$$= X'YZ + XY'Z' + XY'Z + XYZ' + X'YZ$$

$$= \sum_{X,Y,Z} (3,4,5,6,7)$$

### 3. Boolean Algebra

- Examples (2) -

- Ex.3: Derive the product-of-maxterms form for  $H = X' \cdot Y' + X \cdot Z$ .  

$$H = X'Y' + XZ$$

$$= (X'Y'+X)(X'Y'+Z)$$

$$= (X'+X)(Y'+X)(X'+Z)(Y'+Z)$$

$$= (X+Y')(X'+Z)(Y'+Z)$$
- Each OR term in the expression is missing one variable:
  - $X+Y' = X+Y'+ZZ' = (X+Y'+Z)(X+Y'+Z')$
  - $X'+Z = X'+Z+YY' = (X'+Y+Z)(X'+Y'+Z)$
  - $Y'+Z = Y'+Z+XX' = (X+Y'+Z)(X'+Y'+Z)$
- Finally we combine these terms:  

$$H = (X+Y'+Z)(X+Y'+Z')(X'+Y+Z)(X'+Y'+Z)$$

$$\prod_{X,Y,Z} (2,3,4,6)$$

### 3. Boolean Algebra

- Examples (3) -

- Ex.4: Derive the product-of-maxterms form for  $H = X \cdot Y' + X \cdot Z$ .

X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

- From the table, we obtain:

$$H = \prod_{X,Y,Z} (2,3,4,6)$$

$$H = \sum_{X,Y,Z} (0,1,5,7)$$

- Compare this solution with the solution of ex.3.

- Ex.5: Derive a standard form with a reduced number of operators for  $J = XYZ + XYZ' + XY'Z + X'YZ$ .

$$J = XYZ + XYZ' + XYZ + XY'Z + XYZ + X'YZ$$

$$XY(Z+Z') + X(Y+Y')Z + (X+X')YZ$$

$$XY + XZ + YZ$$