

Sistemas Digitais I

LESI - 2º ano

Lesson 6 - Combinational Design Practices

Prof. João Miguel Fernandes

(miguel@di.uminho.pt)

Dept. Informática



UNIVERSIDADE DO MINHO

ESCOLA DE ENGENHARIA

6. Combinational Practices


- PLDs (1) -

- The first PLDs were Programmable Logic Arrays (PLAs).
- A PLA is a combinational, 2-level AND-OR device that can be programmed to realise any sum-of-products logic expression.
- A PLA is limited by:
 - **the number of inputs (n)**
 - **the number of outputs (m)**
 - **the number of product terms (p)**
- We refer to an “n x m PLA with p product terms”. Usually, $p \ll 2^n$.
- An n x m PLA with p product terms contains p 2n-input AND gates and m p-input OR gates.

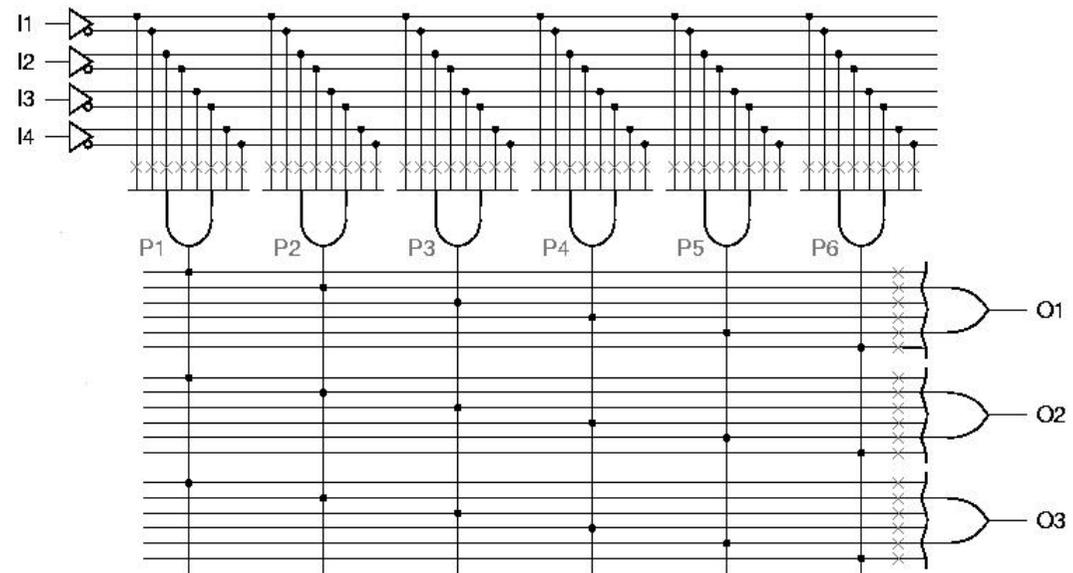6. Combinational Practices

- PLDs (2) -

- Each input is connected to a buffer that produces a true and a complemented version of the signal.
- Potential connections are indicated by Xs.
- The device is programmed by establishing the needed connections.
- The connections are made by fuses.




A 4x3 PLA with 6 product terms.

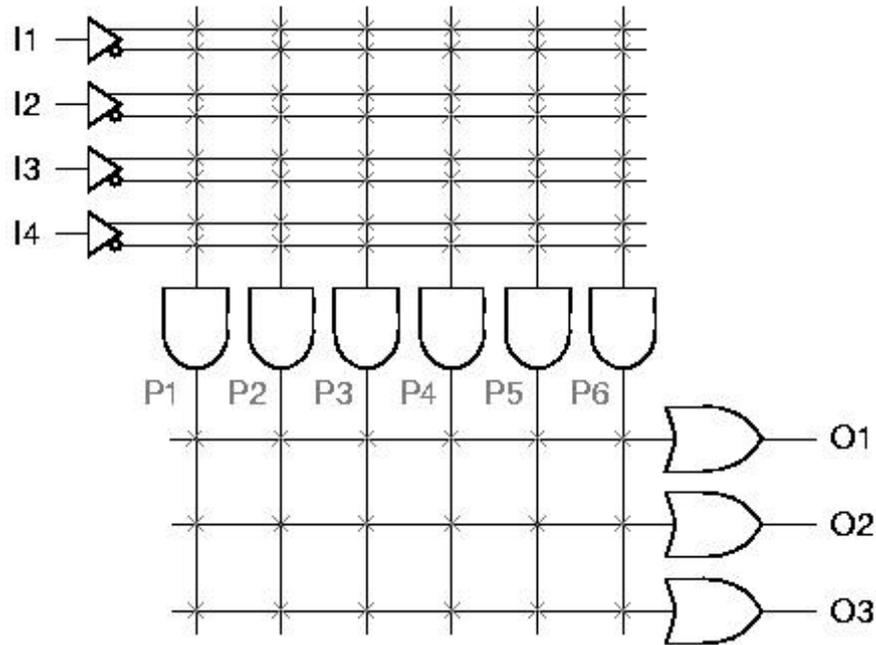
6. Combinational Practices

- PLDs (3) -

- Compact representation of the 4x3 PLA with 6 product terms.



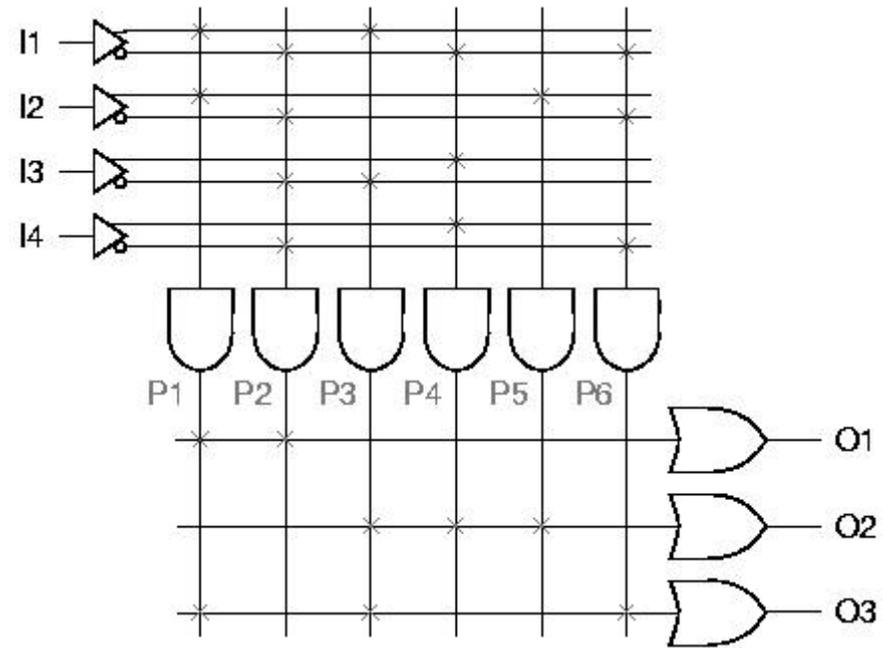
- $O1 = I1 \cdot I2 + I1' \cdot I2' \cdot I3' \cdot I4'$
 $O2 = I1 \cdot I3' + I1' \cdot I3 \cdot I4 + I2$
 $O3 = I1 \cdot I2 + I1 \cdot I3' + I1' \cdot I2' \cdot I4'$



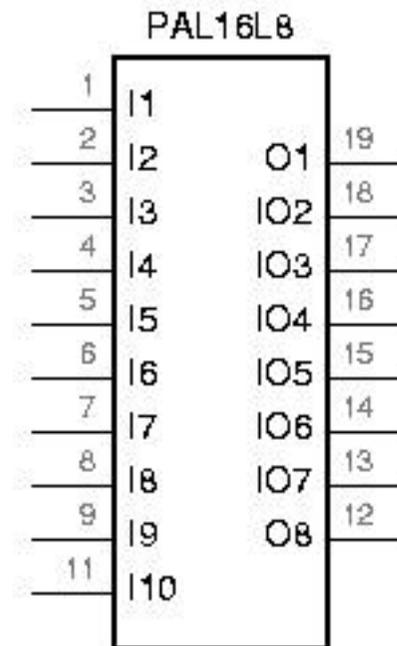6. Combinational Practices

- PLDs (4) -


- Another PLD is PAL (Programmable Array Logic).
- A PAL device has a fixed OR array.
- In a PAL, product terms are not shared by the outputs.
- A PAL is usually faster than a similar PLA.



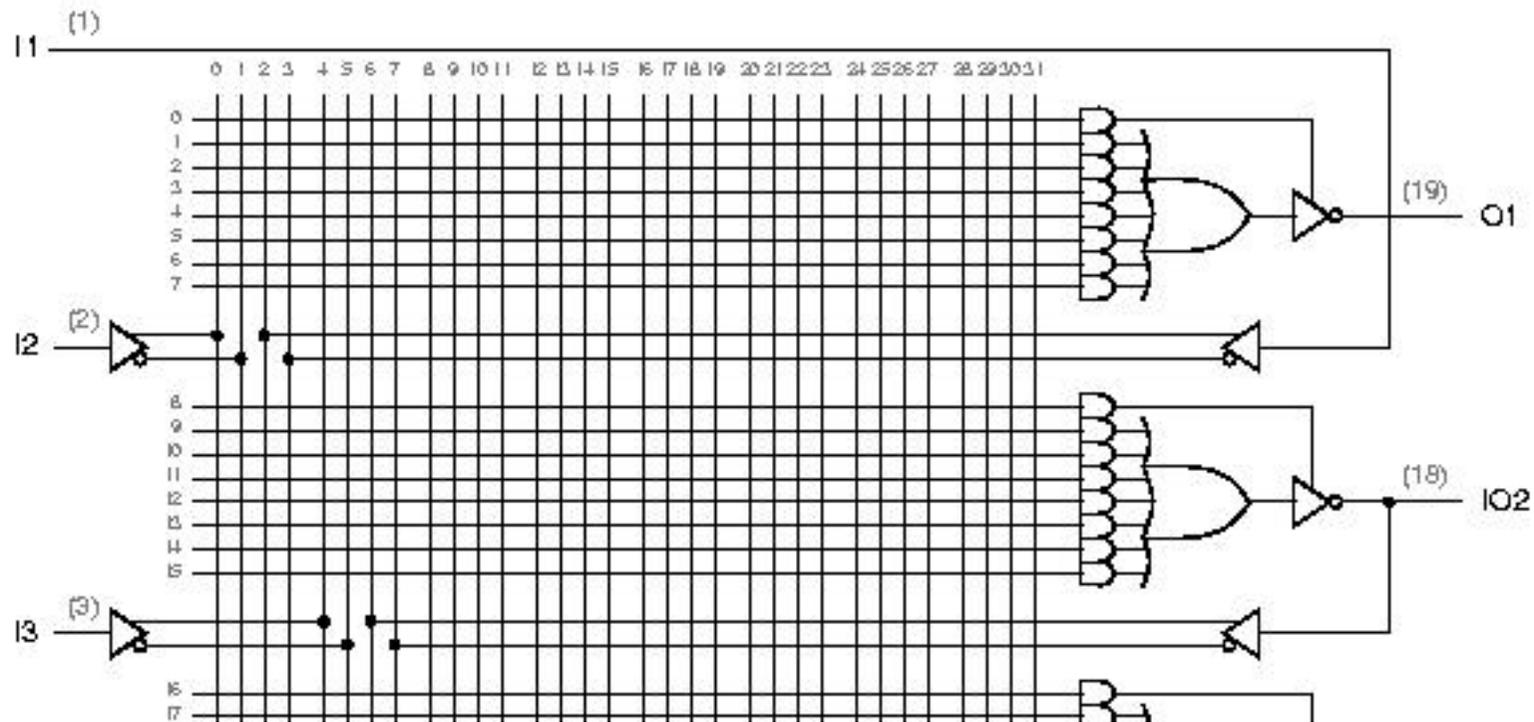6. Combinational Practices

- PLDs (4) -

- Part of the logic diagram of the PAL 16L8.





6. Combinational Practices

- Decoders (1) -

- A decoder is a circuit that converts coded inputs into coded outputs.
- Usually, the input code has fewer bits than the output code.
- The most common decoder is an n-to- 2^n or binary decoder.
- A binary decoder is used when one of 2^n outputs needs to be activated based on an n-bit input value.


Inputs			Outputs			
EN	I1	I0	Y3	Y2	Y1	Y0
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

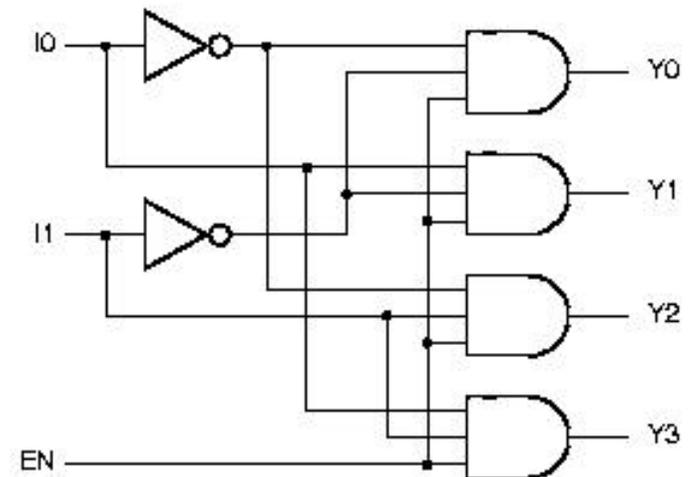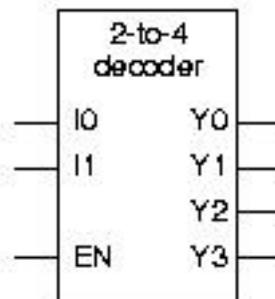

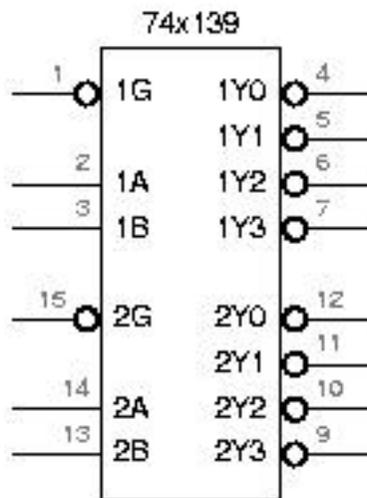6. Combinational Practices

- Decoders (2) -

- A 74x139 IC has two independent 2-to-4 decoders.




inputs			Outputs			
G_L	B	A	Y3_L	Y2_L	Y1_L	Y0_L
1	x	x	1	1	1	1
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1

6. Combinational Practices

- Decoders (3) -

- A 74x138 IC has one 3-to-8 decoder.

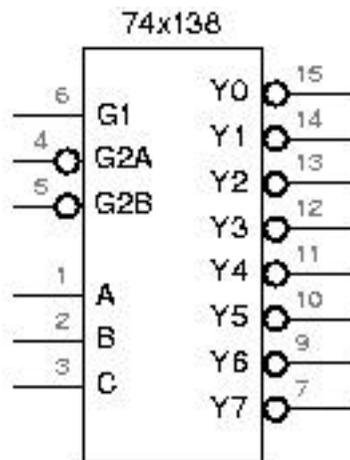


Inputs						Outputs							
G1	G2A_L	G2B_L	C	B	A	Y7_L	Y6_L	Y5_L	Y4_L	Y3_L	Y2_L	Y1_L	Y0_L
0	x	x	x	x	x	1	1	1	1	1	1	1	1
x	1	x	x	x	x	1	1	1	1	1	1	1	1
x	x	1	x	x	x	1	1	1	1	1	1	1	1
1	0	0	0	0	0	1	1	1	1	1	1	1	0
1	0	0	0	0	1	1	1	1	1	1	1	0	1
1	0	0	0	1	0	1	1	1	1	1	0	1	1
1	0	0	0	1	1	1	1	1	1	0	1	1	1
1	0	0	1	0	0	1	1	1	0	1	1	1	1
1	0	0	1	1	0	1	0	1	1	1	1	1	1
1	0	0	1	1	1	0	1	1	1	1	1	1	1

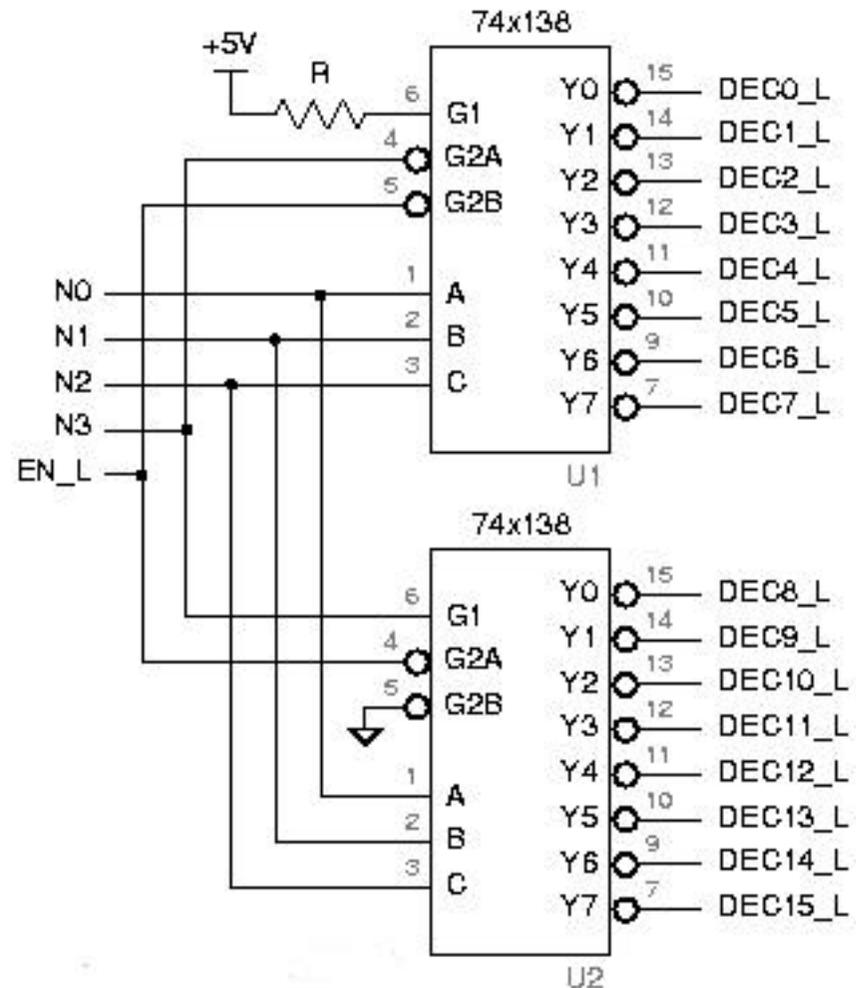6. Combinational Practices

- Decoders (4) -


- Multiple decoders can be used to decode larger code words.
- The top decoder (U1) is enabled when N3 is 0, and the bottom decoder (U2) is enabled when N3 is 1.
- To handle larger code words, decoders can be cascaded hierarchically.



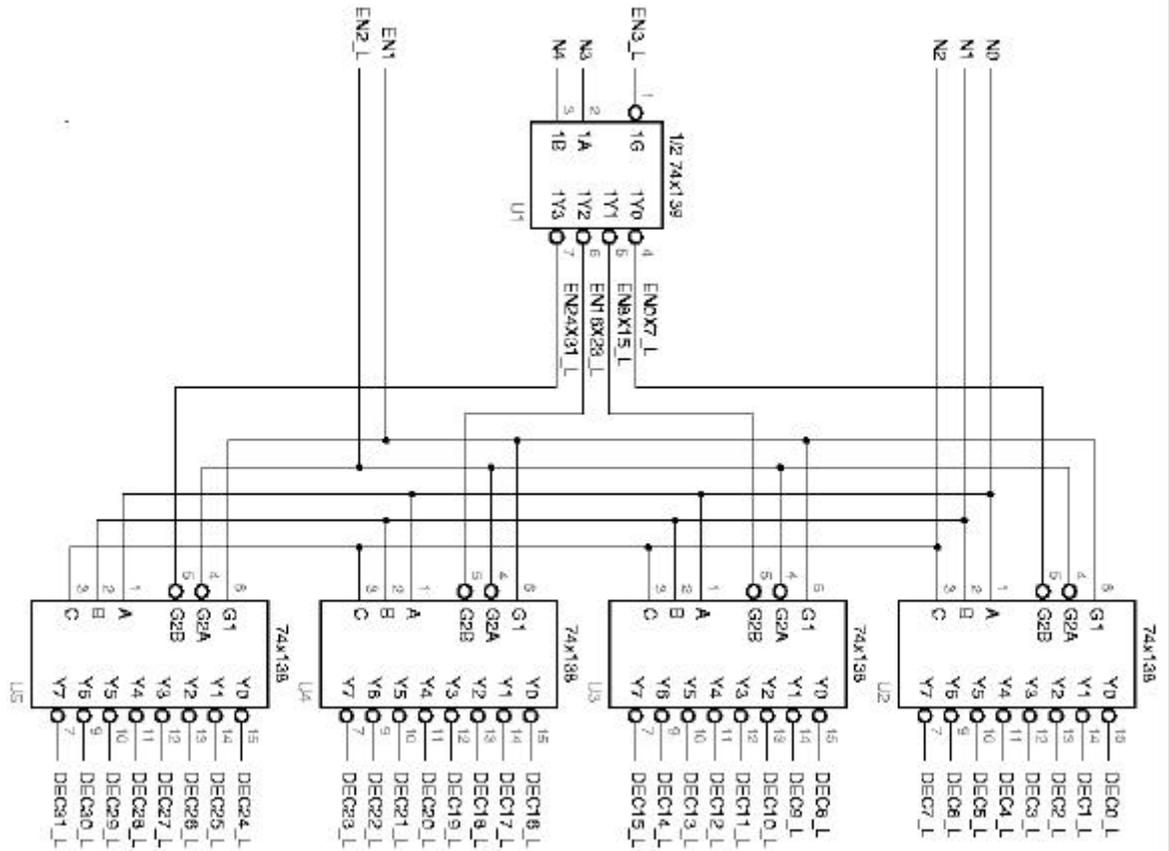6. Combinational Practices

- Decoders (5) -

- To handle larger code words, decoders can be cascaded hierarchically.
- A 5-to-32 decoder can be built with one 2-to-4 and four 3-to-8 decoders.
- The 2-to-4 decoder treats the high order bits.
- The 3-to-8 decoders treat the low-order bits.



6. Combinational Practices

- Decoders (6) -

- There are several ways to write decoders in VHDL.
- The most primitive would be to write a structural description equivalent to the logic circuit on slide 7.

```
library IEEE;
use IEEE.std_logic_1164.all;
entity V2to4dec is
    port (I0, I1, EN: in STD_LOGIC;
          Y0, Y1, Y2, Y3: out STD_LOGIC );
end V2to4dec;
architecture V2to4dec_s of V2to4dec is
    signal NOTI0, NOTI1: STD_LOGIC;
    component inv port (I: in STD_LOGIC; O: out STD_LOGIC ); end component;
    component and3 port (I0, I1, I2: in STD_LOGIC; O: out STD_LOGIC ); end component;
begin
    U1: inv port map (I0,NOTI0);
    U2: inv port map (I1,NOTI1);
    U3: and3 port map (NOTI0,NOTI1,EN,Y0);
    U4: and3 port map ( I0,NOTI1,EN,Y1);
    U5: and3 port map (NOTI0, I1,EN,Y2);
    U6: and3 port map ( I0, I1,EN,Y3);
end V2to4dec_s;
```

6. Combinational Practices

- Decoders (7) -

- The second alternative is using the dataflow style.

```
library IEEE;
use IEEE.std_logic_1164.all;

entity V14x138 is
    port (G1, G2A_L, G2B_L: in STD_LOGIC;           -- enable inputs
          A: in STD_LOGIC_VECTOR (2 downto 0);     -- select inputs
          Y_L: out STD_LOGIC_VECTOR (0 to 7) );    -- decoded outputs
end V14x138;

architecture V14x138_a of V14x138 is
    signal Y_L_i: STD_LOGIC_VECTOR (0 to 7);
begin
    with A select Y_L_i <=
        "01111111" when "000",
        "10111111" when "001",
        "11011111" when "010",
        "11101111" when "011",
        "11110111" when "100",
        "11111011" when "101",
        "11111101" when "110",
        "11111110" when "111",
        "11111111" when others;
    Y_L <= Y_L_i when (G1 and not G2A_L and not G2B_L)='1' else "11111111";
end V14x138_a;
```

6. Combinational Practices

- Decoders (8) -


- Another alternative is using the behavioral style.

```
architecture V3to8dec_c of V3to8dec is
begin
process (G1, G2, G3, A)
  variable i: INTEGER range 0 to 7;
  begin
    Y <= "00000000";
    if (G1 and G2 and G3) = '1' then
      for i in 0 to 7 loop
        if i=CONV_INTEGER(A) then Y(i) <= '1'; end if;
      end loop;
    end if;
  end process;
end V3to8dec_c;
```

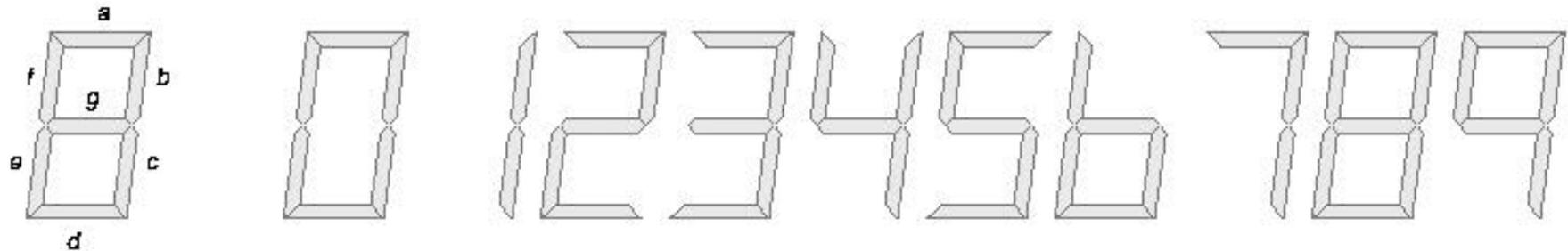6. Combinational Practices

- 7-Segment Decoders (1) -

- A 7-segment display is used in watches, calculators, and devices to show decimal data.
- A digit is displayed by illuminating a subset of the 7 line segments.



- A 7-segment decoder has a 4-bit BCD as its input and the 7-segment code as its output.

6. Combinational Practices

- 7-Segment Decoders (2) -

Inputs					Outputs						
BI_L	D	C	B	A	a	b	c	d	e	f	g
0	x	x	x	x	0	0	0	0	0	0	0
1	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
1	0	0	1	0	1	1	0	1	1	0	1
1	0	0	1	1	1	1	1	1	0	0	1
1	0	1	0	0	0	1	1	0	0	1	1
1	0	1	0	1	1	0	1	1	0	1	1
1	0	1	1	0	0	0	1	1	1	1	1
1	0	1	1	1	1	1	1	0	0	0	0
1	1	0	0	0	1	1	1	1	1	1	1
1	1	0	0	1	1	1	1	0	0	1	1
1	1	0	1	0	0	0	0	1	1	0	1
1	1	0	1	1	0	0	1	1	0	0	1
1	1	1	0	0	0	1	0	0	0	1	1
1	1	1	0	1	1	0	0	1	0	1	1
1	1	1	1	0	0	0	0	1	1	1	1
1	1	1	1	1	0	0	0	0	0	0	0

- Exercise 1:
Obtain minimised expressions for outputs of the 7-segment decoder.
- Exercise 2:
Write a VHDL description of a 7-segment decoder.

6. Combinational Practices

- Encoders (1) -

- An encoder is a circuit whose output code has normally fewer bits than its input code.
- The simplest encoder to build is a 2^n -to- n or binary encoder. It has the opposite function as a binary decoder.


- Equations for an 8-to-3 encoder :

$$Y_0 = I_1 + I_3 + I_5 + I_7$$

$$Y_1 = I_2 + I_3 + I_6 + I_7$$

$$Y_2 = I_4 + I_5 + I_6 + I_7$$

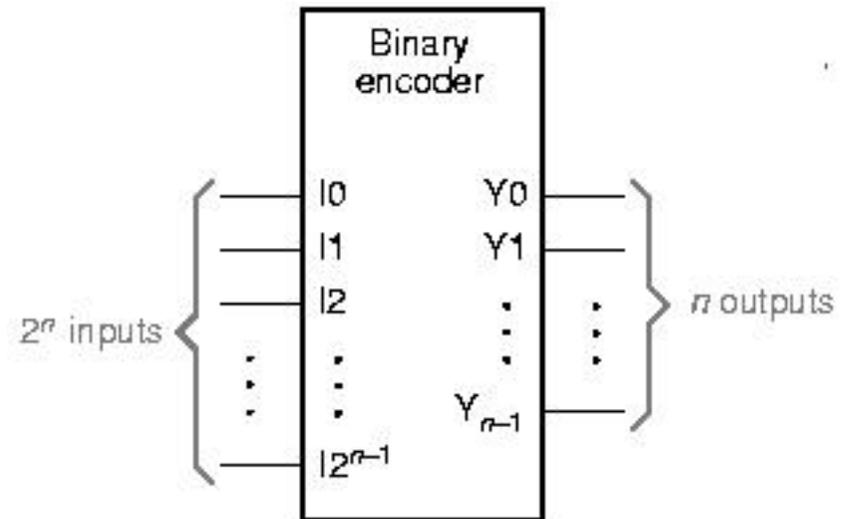
- Only 1 input is active at a time.
What happens if 2 inputs are asserted (ex: I2 and I4)?



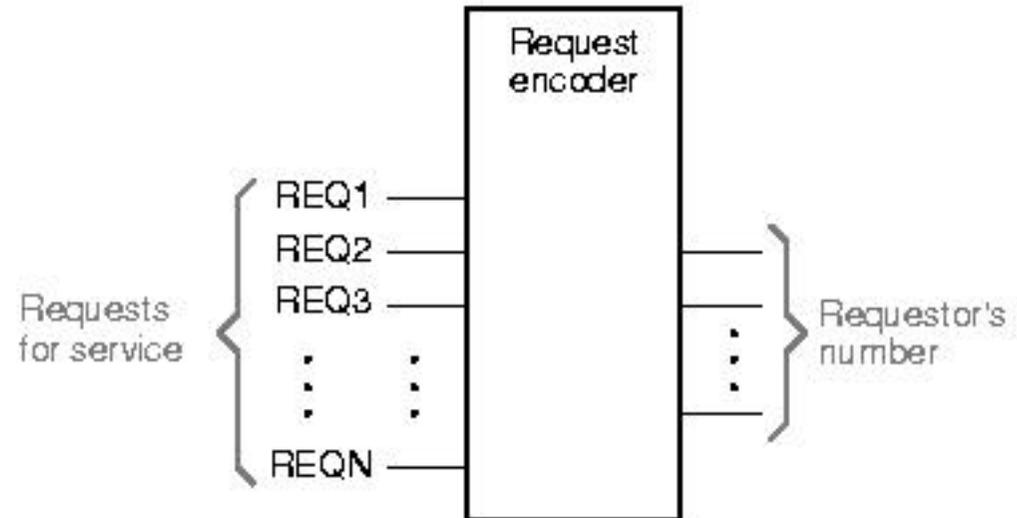6. Combinational Practices

- Encoders (2) -

- To implement a request encoder, the binary encoder does not work!
- It assumes that only 1 input is asserted.




- If multiple requests can be made simultaneously, a priority must be assigned to the input lines.
- When multiple requests are made, the device (priority encoder) produces the number of the highest-priority requestor.

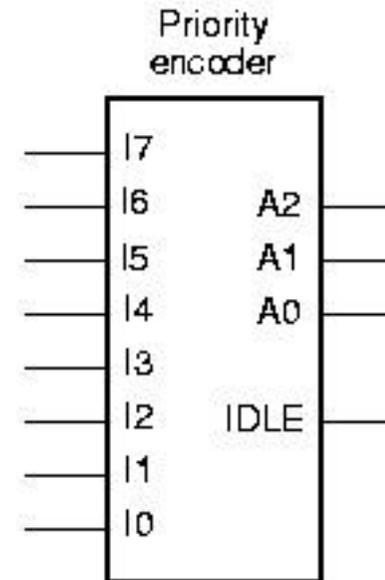6. Combinational Practices

- Encoders (3) -

- Input I7 has the highest priority.
- Outputs A2-A0 contain the number of the highest-priority asserted input, if any.
- The IDLE output is asserted if no inputs are asserted.
- Intermediate variable H_i is 1, if I_i is the highest priority 1-input:
 $H_7 = I_7$ $H_6 = I_6 \cdot I_7'$
 $H_5 = I_5 \cdot I_6' \cdot I_7'$ $H_4 = I_4 \cdot I_5' \cdot I_6' \cdot I_7'$
... (similar equations for H_3 - H_0)




- $A_0 = H_1 + H_3 + H_5 + H_7$
 $A_1 = H_2 + H_3 + H_6 + H_7$
 $A_2 = H_4 + H_5 + H_6 + H_7$
- $IDLE = I_0' \cdot I_1' \cdot I_2' \cdot I_3' \cdot I_4' \cdot I_5' \cdot I_6' \cdot I_7'$

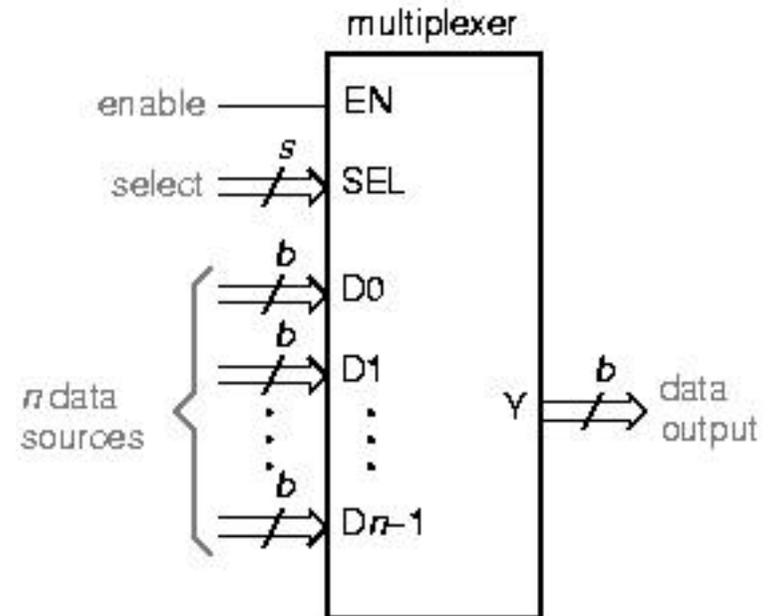6. Combinational Practices

- Multiplexers (1) -


- A multiplexer (mux) is a digital switch.
- It connects data from one of n sources to its output.
- The SEL input selects among the n sources, so $s = \lceil \log_2 n \rceil$.
- When $EN=0$, $Y=0$;
When $EN=1$, the mux is working.
- Multiplexers are used in computers between the processor's registers and its ALU, to select among a set of registers which one is connected to the ALU.



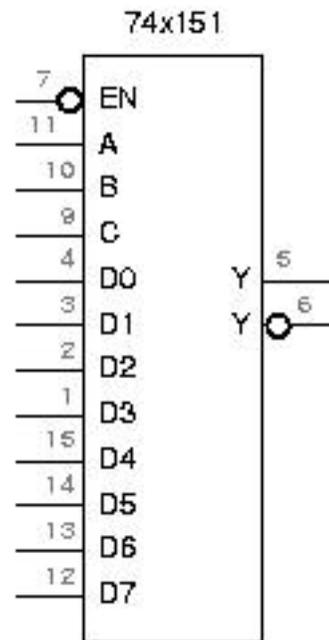6. Combinational Practices

- Multiplexers (2) -

- A 74x151 IC has one 8-input, 1-bit multiplexer.
- The select inputs are named A,B,C, where C is the MSB.
- The enable input EN_L is active low.
- Both active-low and high versions of the output are provided




Inputs				Outputs	
EN_L	C	B	A	Y	Y_L
1	X	X	X	0	1
0	0	0	0	D0	D0'
0	0	0	1	D1	D1'
0	0	1	0	D2	D2'
0	0	1	1	D3	D3'
0	1	0	0	D4	D4'
0	1	0	1	D5	D5'
0	1	1	0	D6	D6'
0	1	1	1	D7	D7'

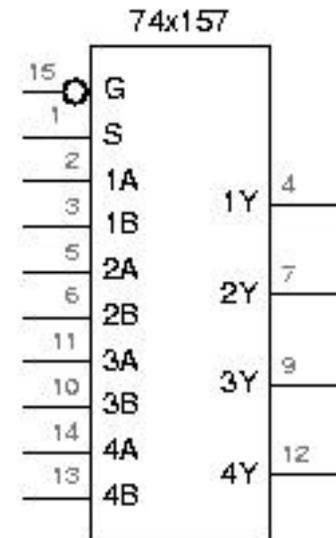6. Combinational Practices

- Multiplexers (3) -

- A 74x157 IC has one 2-input, 4-bit multiplexer.
- The select input is S.
- The enable input G_L is active low.
- The truth table was extended and inputs appear at the outputs columns.





Inputs		Outputs			
G_L	S	1Y	2Y	3Y	4Y
1	X	0	0	0	0
0	0	1A	2A	3A	4A
0	1	1B	2B	3B	4B

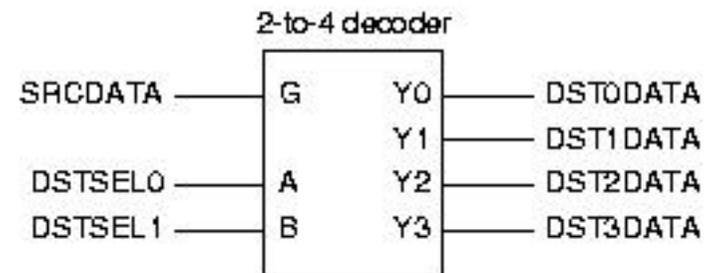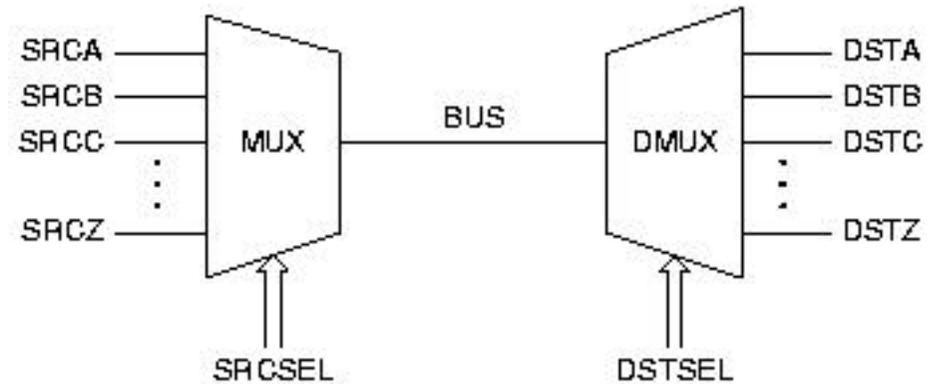6. Combinational Practices

- Multiplexers (4) -

- A multiplexer can be used to select one of n sources of data to transmit on a bus.
- At the other end, a demultiplexer can be used to route the bus to one of m destinations.
- The function of a multiplexer is the inverse of a demultiplexer's.
- A 1-bit, n -output demultiplexer has one data input and s inputs to select one of the $n=2^s$ data outputs.



6. Combinational Practices

- Multiplexers (5) -

- It is easy to describe multiplexers in VHDL.
- In the dataflow style, a `SELECT` statement is required.

```
library IEEE;
use IEEE.std_logic_1164.all;

entity mux4toE is
  port (
    S: in STD_LOGIC_VECTOR (1 downto 0);      -- Select inputs, 0-3 ==> A-D
    A, B, C, D: in STD_LOGIC_VECTOR (1 to E); -- Data bus input
    Y: out STD_LOGIC_VECTOR (1 to E)         -- Data bus output
  );
end mux4toE;

architecture mux4toE of mux4toE is
begin
  with S select Y <=
    A when "00",
    B when "01",
    C when "10",
    D when "11",
    (others => 'U') when others; -- this creates an E-bit vector of 'U'
end mux4toE;
```

6. Combinational Practices

- Multiplexers (6) -

- In a behavioural architecture, a `CASE` statement is used.

```
architecture mux4in8p of mux4in8b is
begin
process(S, A, B, C, D)
begin
case S is
when "00" => Y <= A;
when "01" => Y <= B;
when "10" => Y <= C;
when "11" => Y <= D;
when others => Y <= (others => 'U'); -- B-bit vector of 'U'
end case;
end process;
end mux4in8p;
```

- It is easy to customise the selection criteria in a VHDL multiplexer program.

6. Combinational Practices

- XOR and Parity Circuits (1) -


- An Exclusive-OR (XOR) gate is a 2-input gate whose output is 1, if exactly one of its inputs is 1.
- An XOR gate produces a 1 output if its input are different.
- An Exclusive-NOR (XNOR) is just the opposite: it produces a 1 output if its inputs are the same.
- The XOR operation is denoted by the symbol \oplus .
- $X \oplus Y = X' \cdot Y + X \cdot Y'$

X	Y	$X \oplus Y$ (XOR)	$(X \oplus Y)$ (XNOR)
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

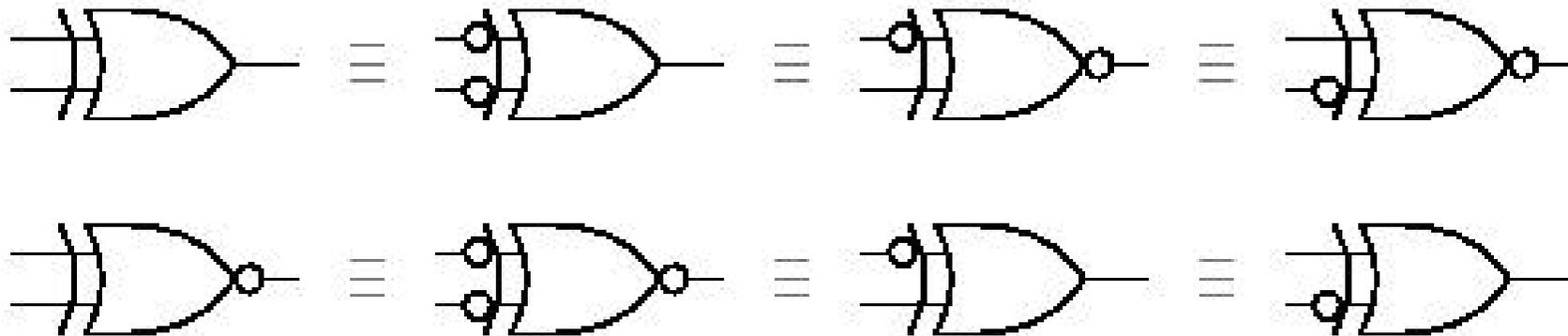6. Combinational Practices

- XOR and Parity Circuits (2) -

- There are 4 symbols for each XOR and XNOR function.





- These alternatives are a consequence of the following rule:
 - Any two signals (inputs or output) of an XOR or XNOR gate may be complemented without changing the resulting logic function.**
- In bubble-to-bubble design we choose the symbol that is most expressive of the logic function being performed.

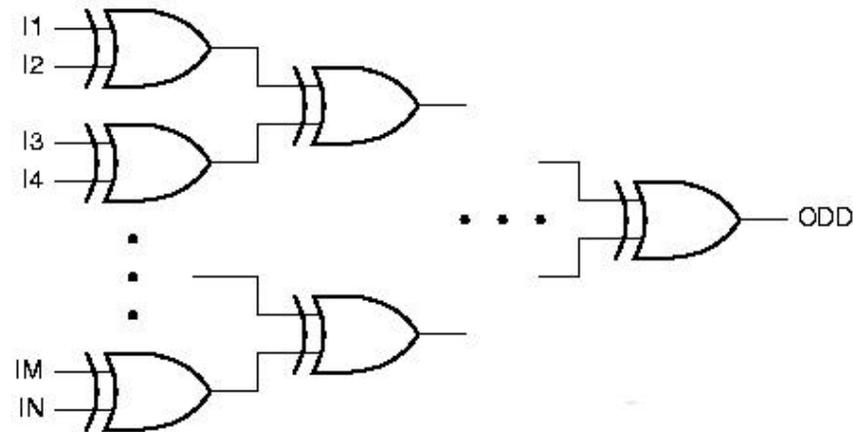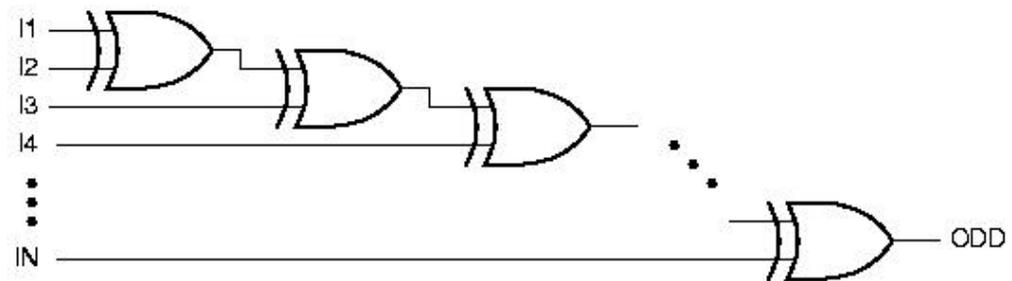6. Combinational Practices

- XOR and Parity Circuits (3) -

- n XOR gates may be cascaded to form a circuit with $n+1$ inputs and a single output. This is a odd-parity circuit, because its output is 1 if an odd number of its inputs are 1.
- If the output of either circuit is inverted, we get an even-parity circuit, whose output is 1 if an even number of its inputs are 1.



6. Combinational Practices

- XOR and Parity Circuits (4) -

- VHDL provides the primitive operators `xor` and `xnor`.
- A 3-input XOR device can be specified in VHDL dataflow style program.

```
library IEEE;
use IEEE.std_logic_1164.all;
entity vxor3 is
    port (A, B, C: in STD_LOGIC;
          Y: out STD_LOGIC);
end vxor3;

architecture vxor3 of vxor3 is
begin
    Y <= A xor B xor C;
end vxor3;
```

6. Combinational Practices

- XOR and Parity Circuits (5) -

- A 9-input parity function can be specified behaviourally.

```
library IEEE;
use IEEE.std_logic_1164.all;

entity parity9 is
    port (I: in STD_LOGIC_VECTOR (1 to 9);
          EVEN, ODD: out STD_LOGIC);
end parity9;

architecture parity9p of parity9 is
begin
    process (I)
        variable p : STD_LOGIC;
    begin
        p := I(1);
        for j in 2 to 9 loop
            if I(j) = '1' then p := not p; end if;
        end loop;
        ODD <= p;
        EVEN <= not p;
    end process;
end parity9p;
```

6. Combinational Practices

- Comparators (1) -


- Comparing two binary words is a common operation in computers.
- A circuit that compares 2 binary words and indicates whether they are equal is a comparator.
- Some comparators interpret their input as signed or unsigned numbers and also indicate an arithmetic relationship (greater or less than) between the words.
- These circuits are often called magnitude comparators.
- XOR and XNOR gates can be viewed as 1-bit comparators.
- The DIFF output is asserted if the inputs are different.



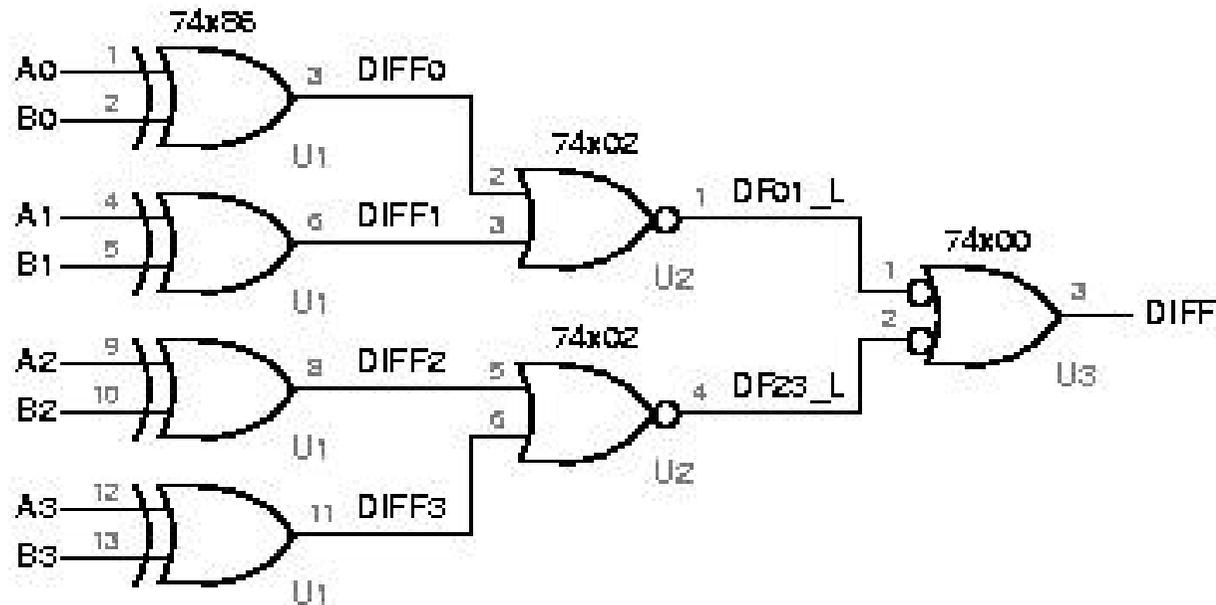6. Combinational Practices

- Comparators (2) -

- The outputs of 4 XOR gates can be ORed to create a 4-bit comparator.




- The DIFF output is asserted if any of the input-bit pairs are different.
- This circuit can be easily adapted to any number of bits per word.

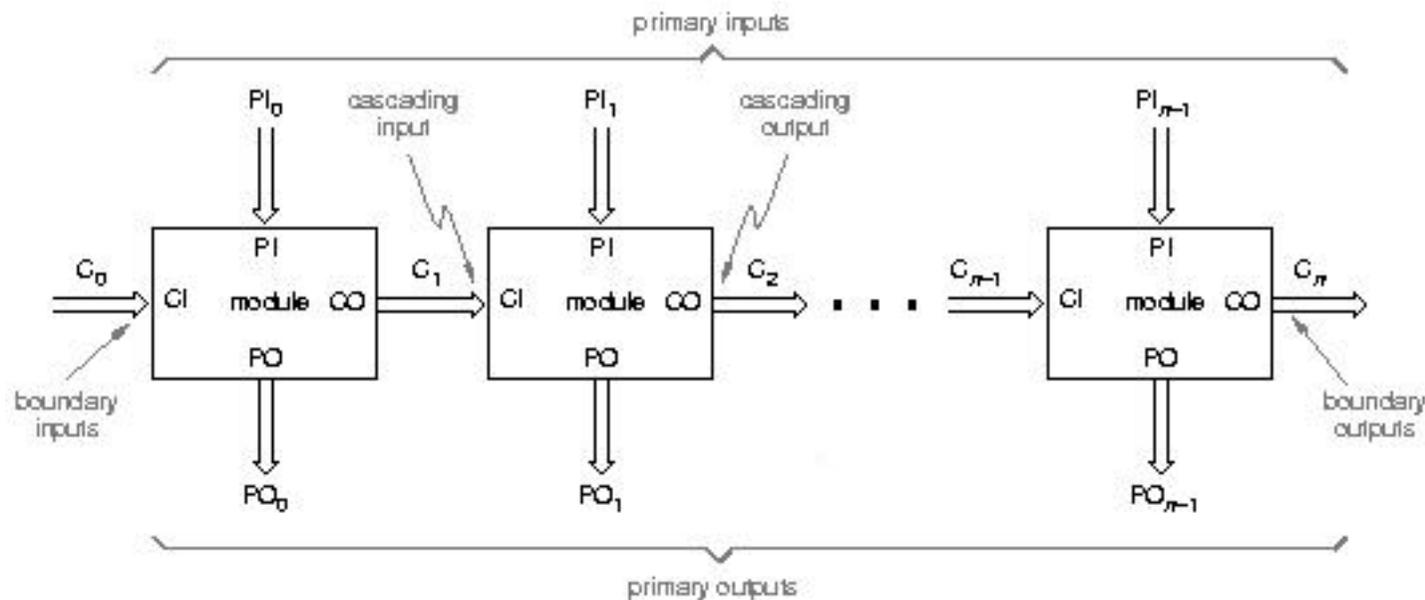6. Combinational Practices

- Comparators (3) -

- An iterative circuit is a combinational circuit with the following structure.





- The circuit contains n identical modules, each of which has both primary inputs and outputs and cascading inputs and outputs.
- The left-most cascading inputs are usually connected to fixed values.

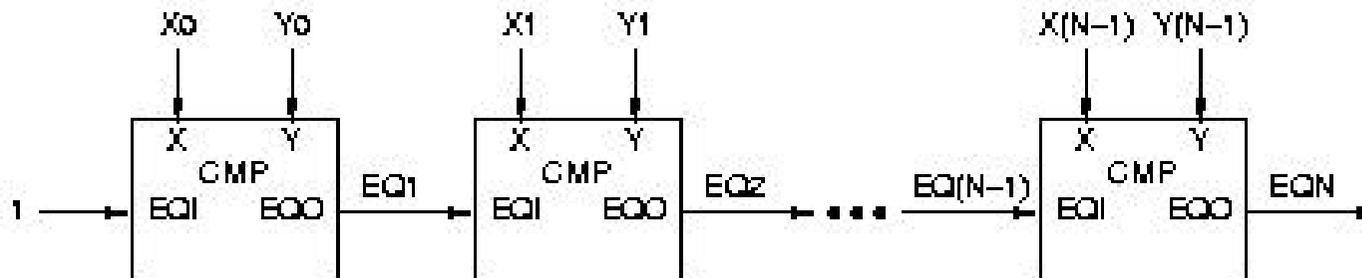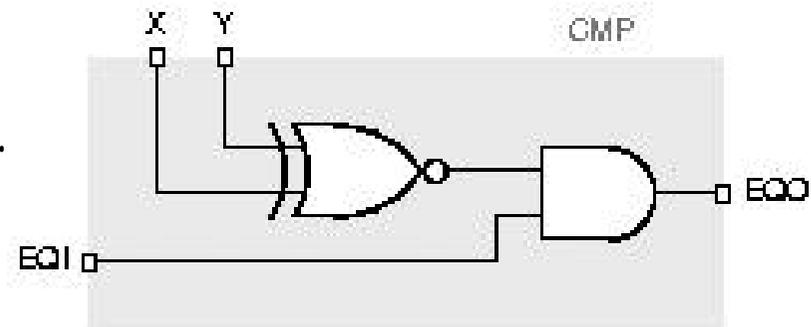6. Combinational Practices

- Comparators (4) -


- Two n -bit values X and Y can be compared one bit at a time using a single bit EQ_i at each step to keep track of whether all of the bit-pairs have been equal so far:
- 1. Set EQ_0 to 1 and set i to 0.
- 2. If EQ_i is 1 and $X_i=Y_i$, set EQ_{i+1} to 1. Else set EQ_{i+1} to 0.
- 3. Increment i .
- 4. If $i < n$, go to step 2.



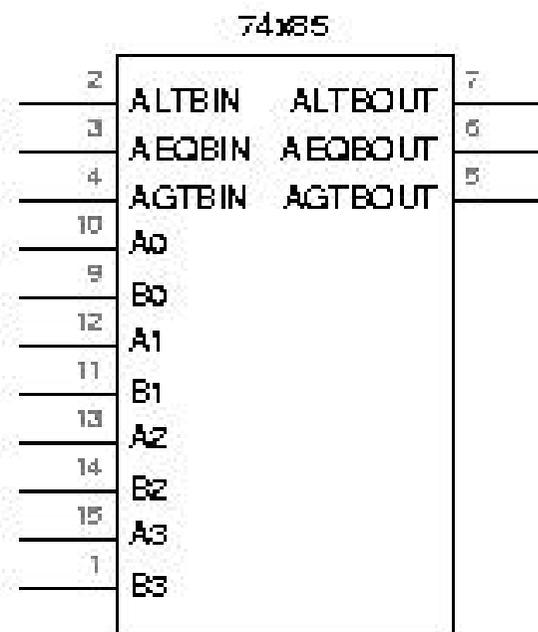6. Combinational Practices

- Comparators (5) -


- Several MSI comparators have been developed commercially.
- The 74x85 is a 4-bit comparator.
- It provides a greater-than output, a less-than output and an equal output.
- The 74x85 also has cascading inputs for combining multiple chips to create comparators for more than 4 bits.
- $AGTBOUT = (A > B) + (A = B) \cdot AGTBIN$
 $AEQBOUT = (A = B) \cdot AEQBIN$
 $ALTBOUT = (A < B) + (A = B) \cdot ALTBIN$



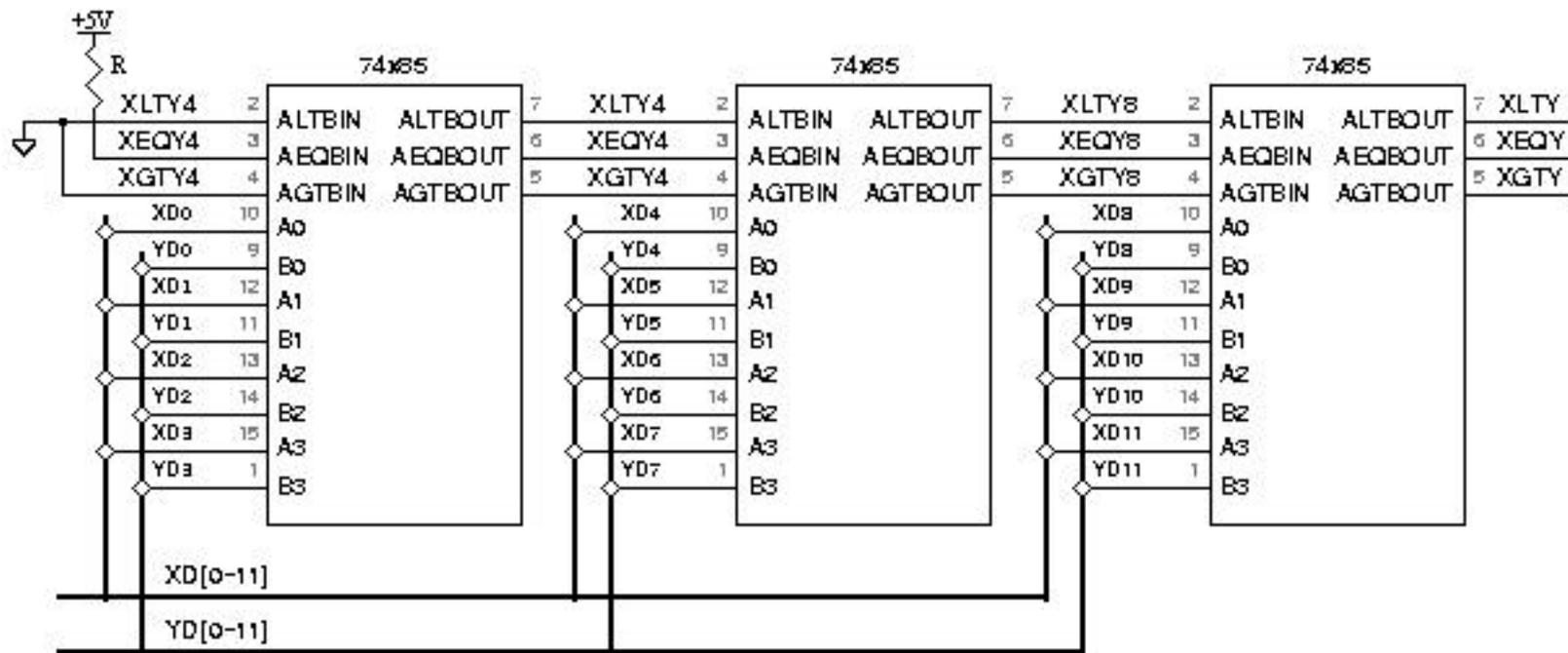6. Combinational Practices

- Comparators (6) -

- With three 74x85 circuits, a 12-bit comparator can be built.



6. Combinational Practices

- Comparators (7) -

- VHDL has comparison operators for all of its built-in types.
- Equality (=) and inequality (/=) operators apply to all types.
- For array and record types, the operands must have equal size and structure, and the operands are compared component by component.
- VHDL's other comparison operators (>, <, >=, <=) apply only to integers, enumerated types and one-dimensional arrays of enumeration or integer types.

6. Combinational Practices

- Adders, Subtractors and ALUs (1) -

- Addition is the most commonly performed arithmetic operation in digital systems.
- An adder combines two arithmetic operands using the addition rules.
- The same addition rules, and hence the same adders, are used for both unsigned and 2's complement numbers.
- An adder can perform subtraction as the addition of the minuend and the complemented subtrahend.
- A subtractor can also be built to perform subtraction directly.
- An ALU (Arithmetic and Logic Unit) performs addition, subtraction, and other logical operations.

6. Combinational Practices



- Adders, Subtractors and ALUs (2) -

- The simplest adder, called a half adder, adds two 1-bit operands X and Y, producing a 2-bit sum.
- The sum can range from 0 to 2, which requires two bits to express.
- The low-order bit of the sum may be named HS (half sum).
- The high-order bit of the sum may be named CO (carry out).
- The following equations can be written:
$$HS = X \oplus Y = X \cdot Y' + X' \cdot Y$$
$$CO = X \cdot Y$$
- To add operands with more than one bit, carries between bit positions must be provided.

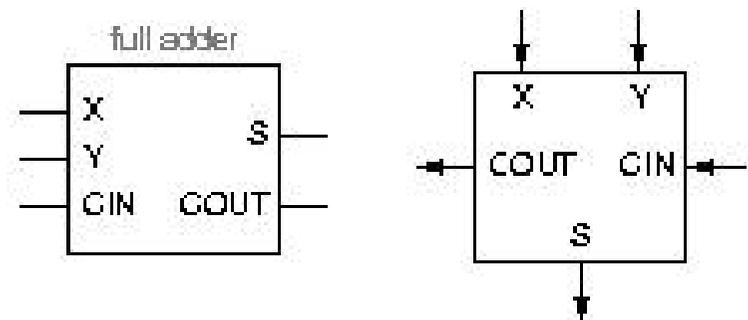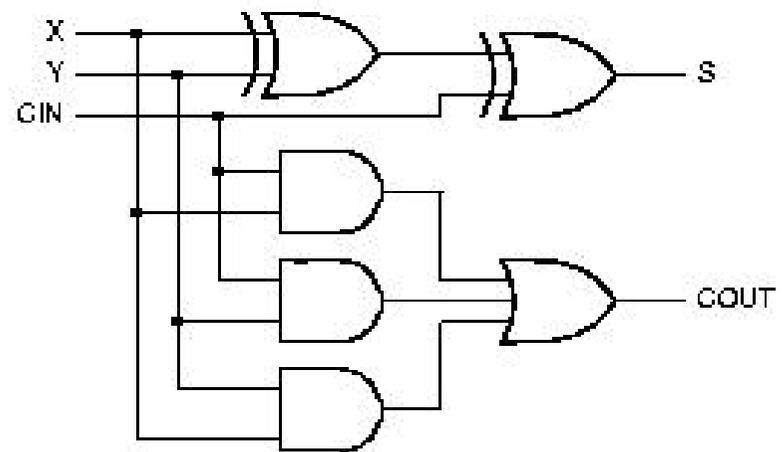6. Combinational Practices

- Adders, Subtractors and ALUs (3) -


- The building block for this operation is called a full adder.
- Besides the addend-bit inputs X and Y, a full adder has a carry-bit input, CIN.
- The sum of the 3 bits can range from 0 to 3, which can still be expressed with just two output bits, S and COUT.
- The following equations can be written:
$$S = X \oplus Y \oplus CIN$$
$$COUT = X \cdot Y + X \cdot CIN + Y \cdot CIN$$



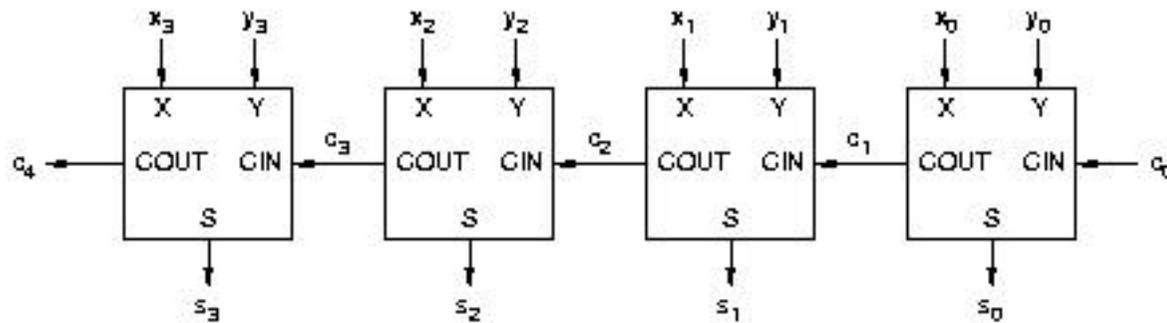6. Combinational Practices

- Adders, Subtractors and ALUs (4) -

- Two binary words, each with n bits, can be added using a ripple adder.
- A ripple adder is a cascade of n full-adders stages, each of which handles one bit.



- The carry input to the least significant bit (c_0) is usually set to 0.
- The carry output of each full adder is connected to the carry input of the next most significant full adder.


6. Combinational Practices

- Adders, Subtractors and ALUs (5) -

- The binary subtraction operation is analogous to binary addition.
- A full subtractor has inputs X (minuend), Y (subtrahend) and BIN (borrow in) and outputs D (difference) and BOUT (borrow out).
- The following equations can be written:
$$D = X \oplus Y \oplus \text{BIN}$$
$$\text{BOUT} = X' \cdot Y + X' \cdot \text{BIN} + Y \cdot \text{BIN}$$
- These equations are similar to the equations for a full adder.
$$D = X \oplus Y' \oplus \text{BIN}'$$
$$\text{BOUT} = X \cdot Y' + X \cdot \text{BIN}' + Y' \cdot \text{BIN}'$$
- A full subtractor can be built from a full adder. $X - Y = X + Y' + 1$

6. Combinational Practices


- Adders, Subtractors and ALUs (6) -

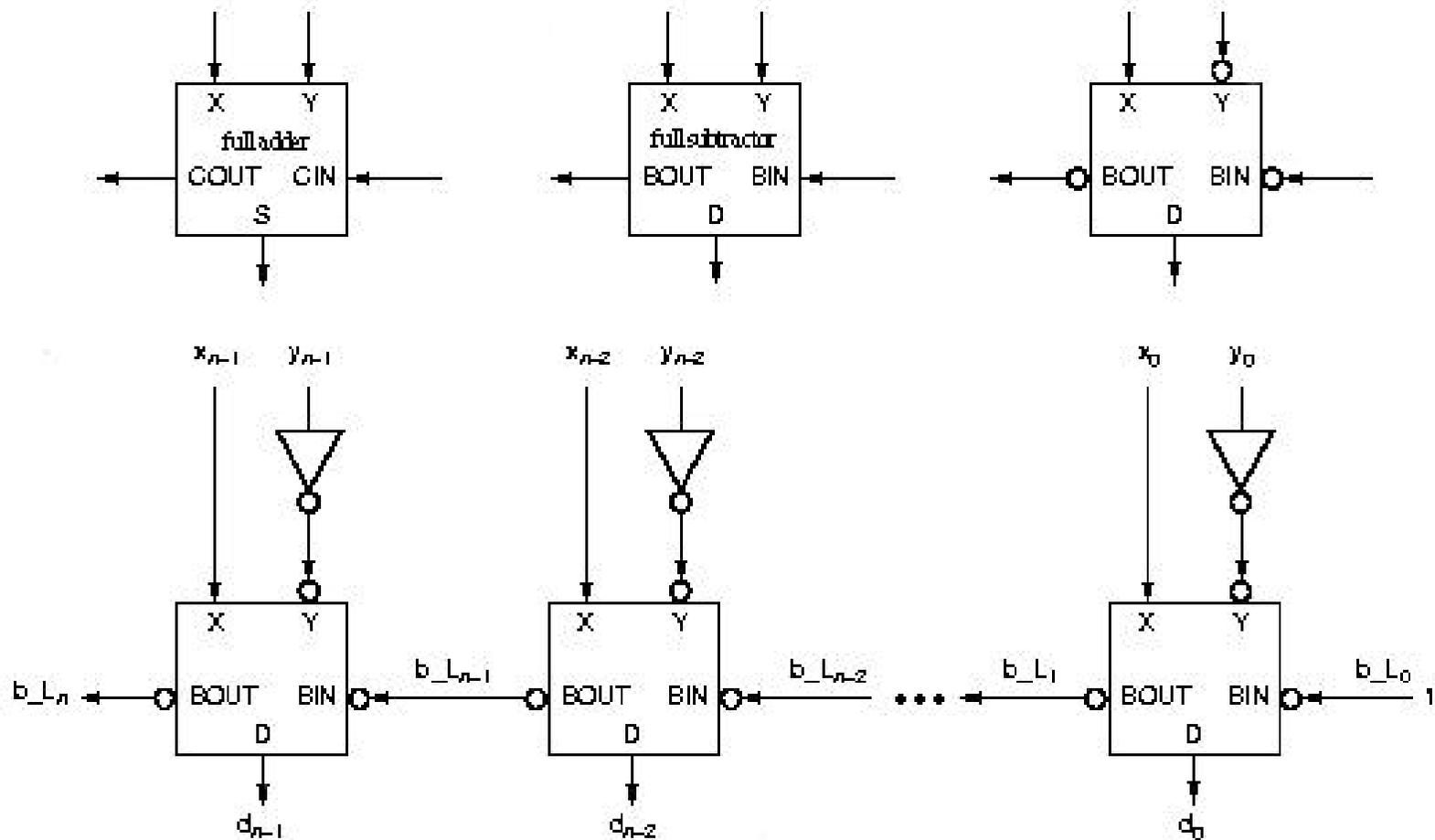

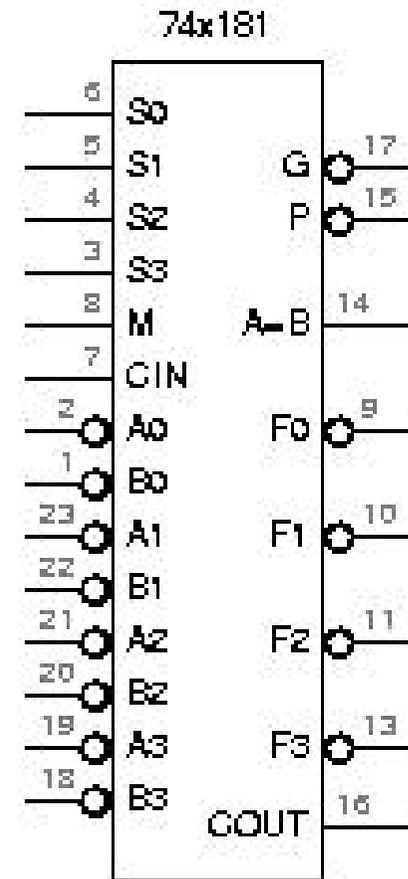6. Combinational Practices

- Adders, Subtractors and ALUs (7) -

- An ALU is a combinational circuit that can perform several arithmetic and logical operations on a pair of b-bit operands.
- The operation to be performed is specified by a set of function-select inputs.
- Typical MSI ALUs have 4-bit operands and three to five function-select inputs, allowing up to 32 different functions to be performed.
- A 74x181 IC has one 4-bit ALU.
- The operation performed by the 74x181 is selected by the M and S3-S0 inputs.



6. Combinational Practices

- Adders, Subtractors and ALUs (8) -

Inputs				Function	
S3	S2	S1	S0	M = 0 (arithmetic)	M = 1 (logic)
0	0	0	0	$F = A \text{ minus } 1 \text{ plus CIN}$	$F = A'$
0	0	0	1	$F = A \cdot B \text{ minus } 1 \text{ plus CIN}$	$F = A' + B'$
0	0	1	0	$F = A \cdot B' \text{ minus } 1 \text{ plus CIN}$	$F = A' + B$
0	0	1	1	$F = 1111 \text{ plus CIN}$	$F = 1111$
0	1	0	0	$F = A \text{ plus } (A + B') \text{ plus CIN}$	$F = A' \cdot B'$
0	1	0	1	$F = A \cdot B \text{ plus } (A + B') \text{ plus CIN}$	$F = B'$
0	1	1	0	$F = A \text{ minus } B \text{ minus } 1 \text{ plus CIN}$	$F = A \oplus B'$
0	1	1	1	$F = A + B' \text{ plus CIN}$	$F = A + B'$
1	0	0	0	$F = A \text{ plus } (A + B) \text{ plus CIN}$	$F = A' \cdot B$
1	0	0	1	$F = A \text{ plus } B \text{ plus CIN}$	$F = A \oplus B$
1	0	1	0	$F = A \cdot B' \text{ plus } (A + B) \text{ plus CIN}$	$F = B$
1	0	1	1	$F = A + B \text{ plus CIN}$	$F = A + B$
1	1	0	0	$F = A \text{ plus } A \text{ plus CIN}$	$F = 0000$
1	1	0	1	$F = A \cdot B \text{ plus } A \text{ plus CIN}$	$F = A \cdot B'$
1	1	1	0	$F = A \cdot B' \text{ plus } A \text{ plus CIN}$	$F = A \cdot B$
1	1	1	1	$F = A \text{ plus CIN}$	$F = A$

6. Combinational Practices

- *Adders, Subtractors and ALUs (9)* -

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;


entity vaddshr is
    port (
        A, B, C, D: in SIGNED (7 downto 0);
        SEL: in STD_LOGIC;
        S: out SIGNED (7 downto 0)
    );
end vaddshr;

architecture vaddshr_arch of vaddshr is
begin
    S <= A + B when SEL = '1' else C + D;
end vaddshr_arch;
```

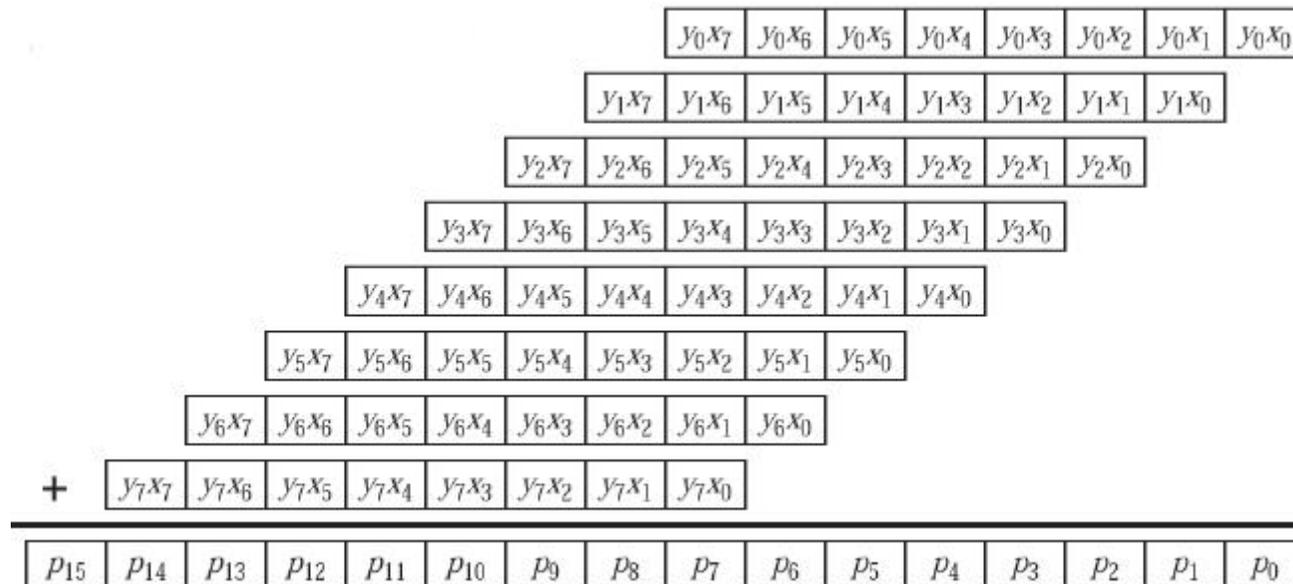6. Combinational Practices


- Multipliers (1) -

- The traditional algorithm to multiply binary numbers uses shifts and adds to obtain the result.
- However, it is not the only solution to implement a multiplier.
- Given 2 n-bit inputs (X, Y), we can write a truth table that expresses the 2n-bit product $P=X \times Y$ as a combinational function of X and Y.
- Most approaches to combinational multipliers are based on the traditional shift-and-add algorithm.



6. Combinational Practices

- Multipliers (2) -

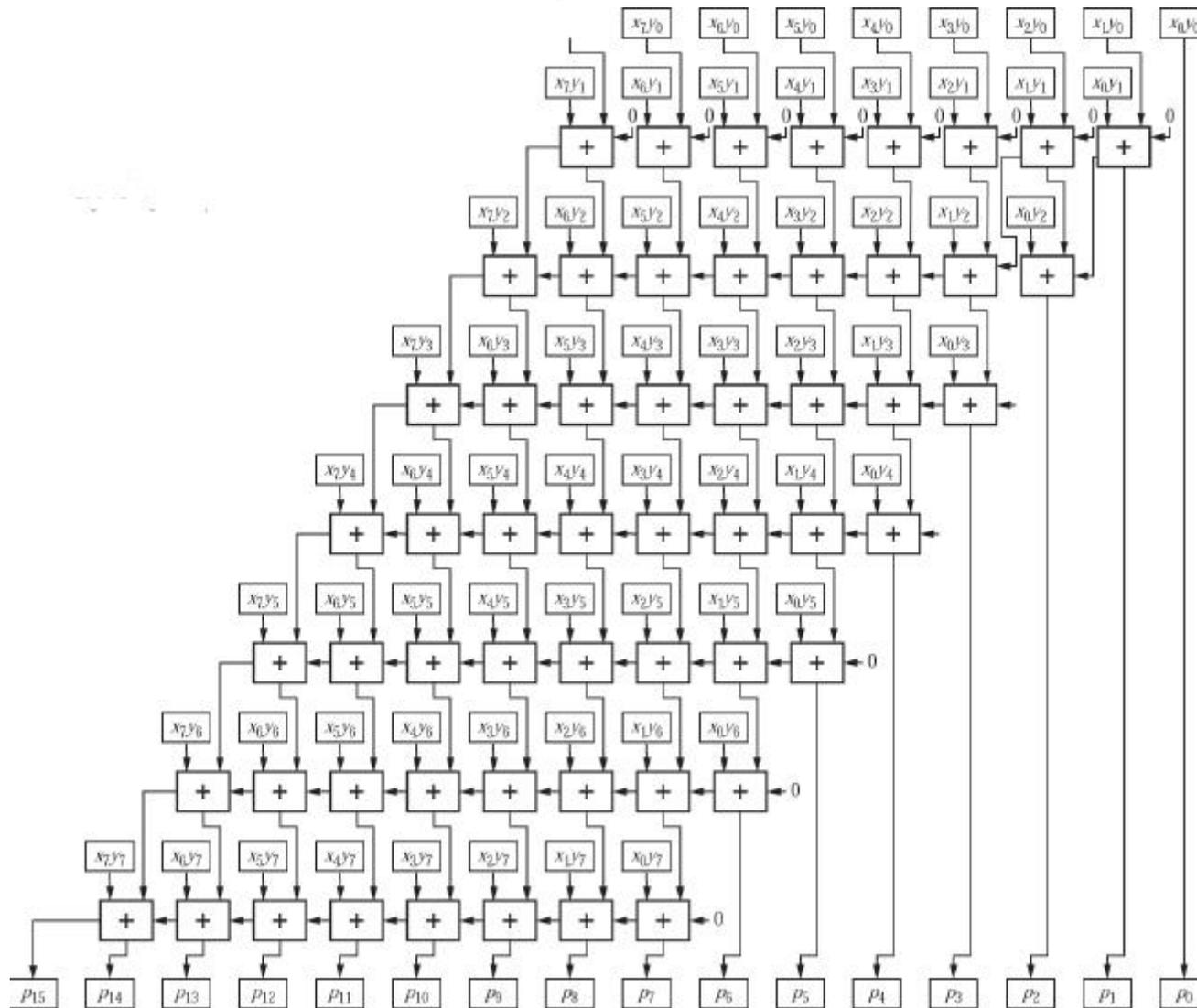

6. Combinational Practices

- Multipliers (3) -

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;

entity vmul8x8i is
    port (
        X: in UNSIGNED (7 downto 0);
        Y: in UNSIGNED (7 downto 0);
        P: out UNSIGNED (15 downto 0)
    );
end vmul8x8i;

architecture vmul8x8i_arch of vmul8x8i is
begin
    P <= X * Y;
end vmul8x8i_arch;
```
